



Transistors

COMP311 Connor McMahon

Announcements

- Homework 0 due tomorrow
- Lab 0 released tomorrow, due next Thursday

Arithmetic vs Logical Shifting

sizeof(int) = 4 bytes

```
unsigned int x3 = (unsigned int) -5;  
printf("x3 >> 1 = 0x%x\n", x3 >> 1);
```

Arithmetic vs Logical Shifting

sizeof(int) = 4 bytes

```
unsigned int x3 = (unsigned int) -5;  
printf("x3 >> 1 = 0x%x\n", x3 >> 1);
```

-5 in binary is $1\dots1011_2$

This is a 32-bit number
because its type is
unsigned int

$1\dots1011_2 \gg 1 = 0111\dots1101_2 = 0x7FFFFFFD$

A logical shift was
performed because this
number is an **unsigned** int

Transistors are like switches




Switches are controlled by physical contact

Transistors are controlled by a **voltage**

Transistor Symbol




Switch

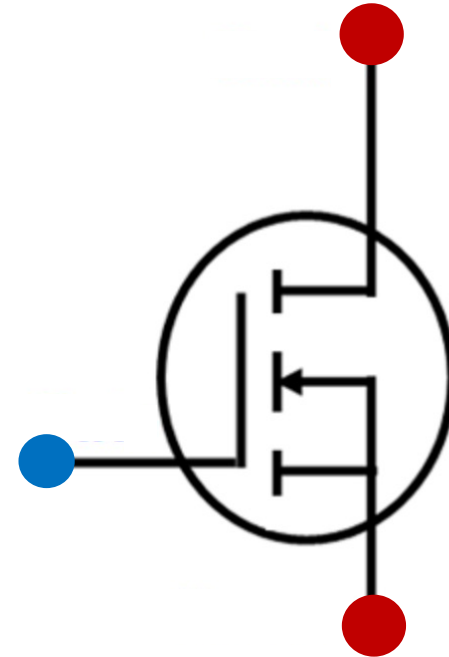


Transistor
(n-channel MOSFET)

Logic Levels

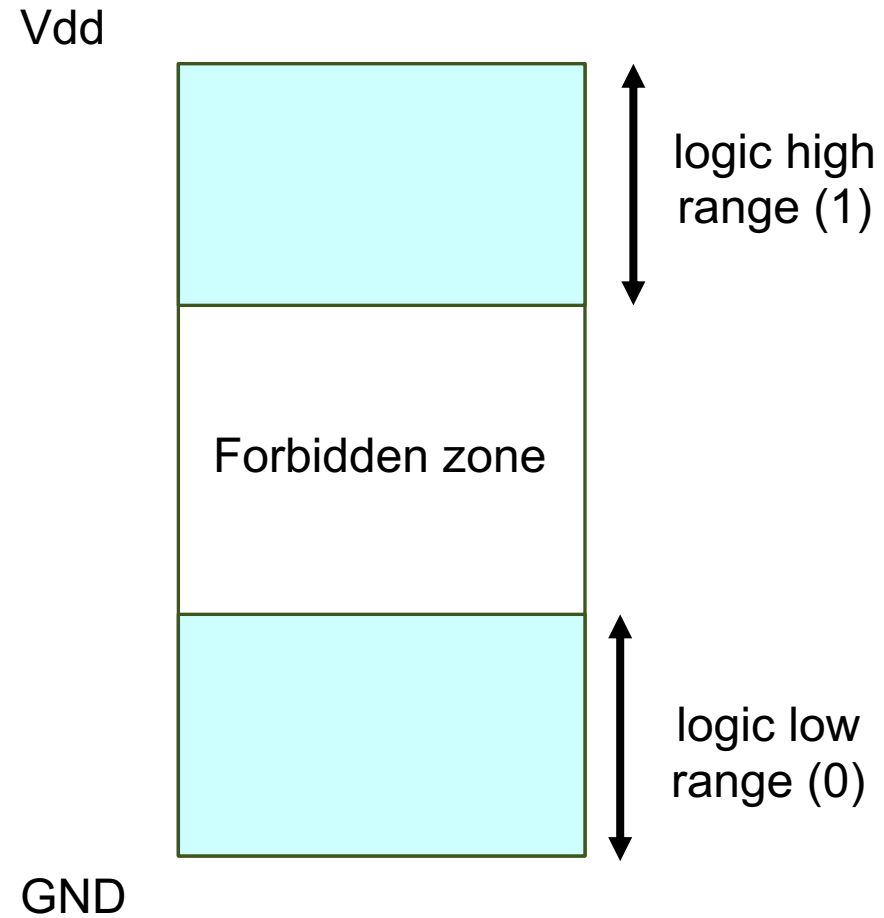



The exact voltage ranges are determined by the characteristics of the transistor

NMOS Transistor

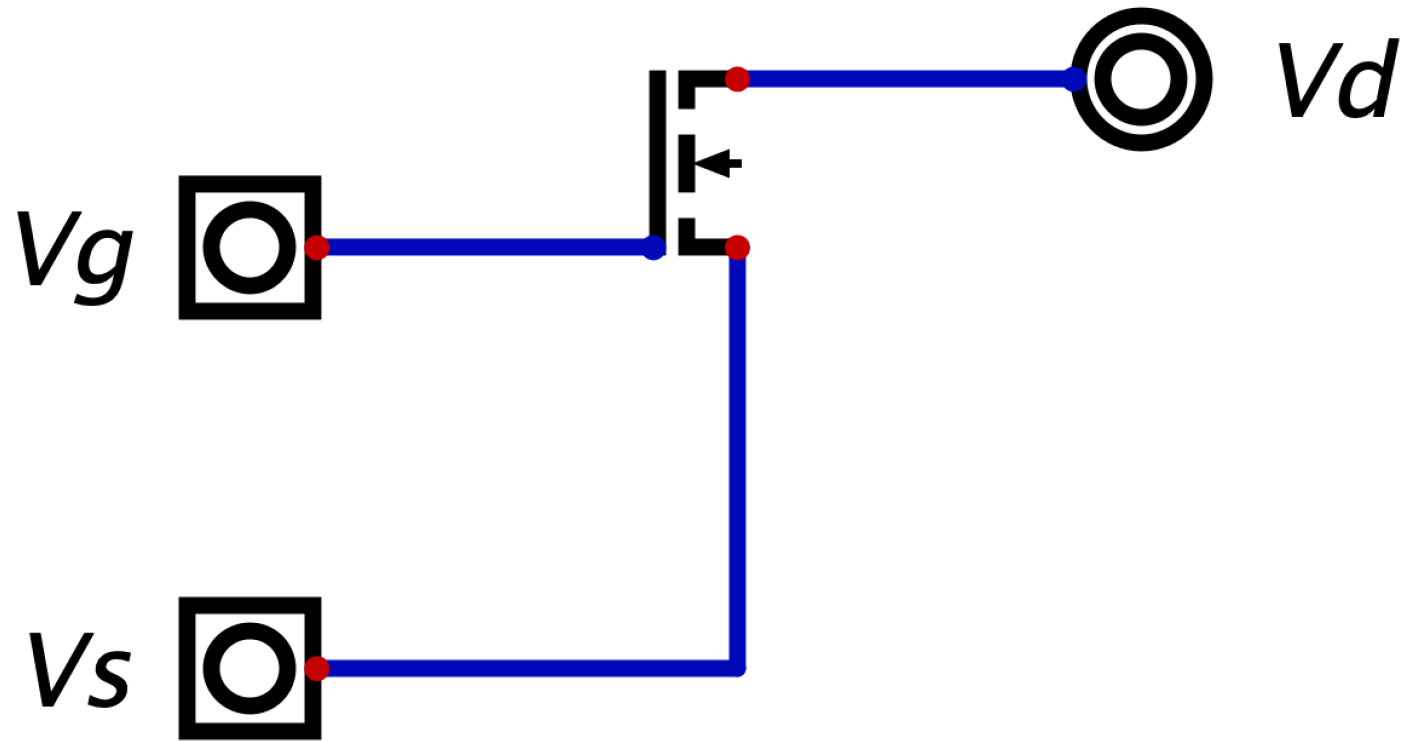

NMOS Transistor in “on” state

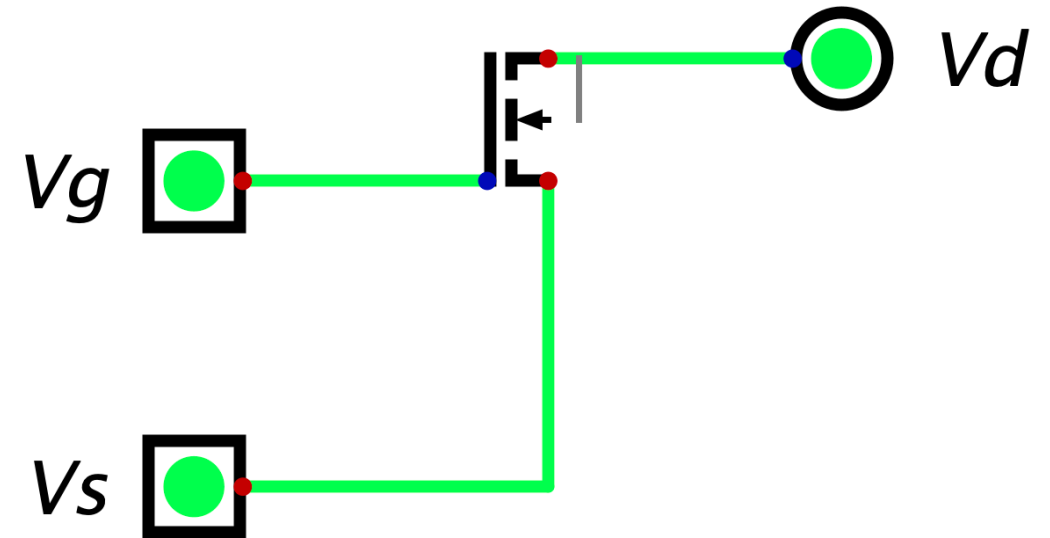
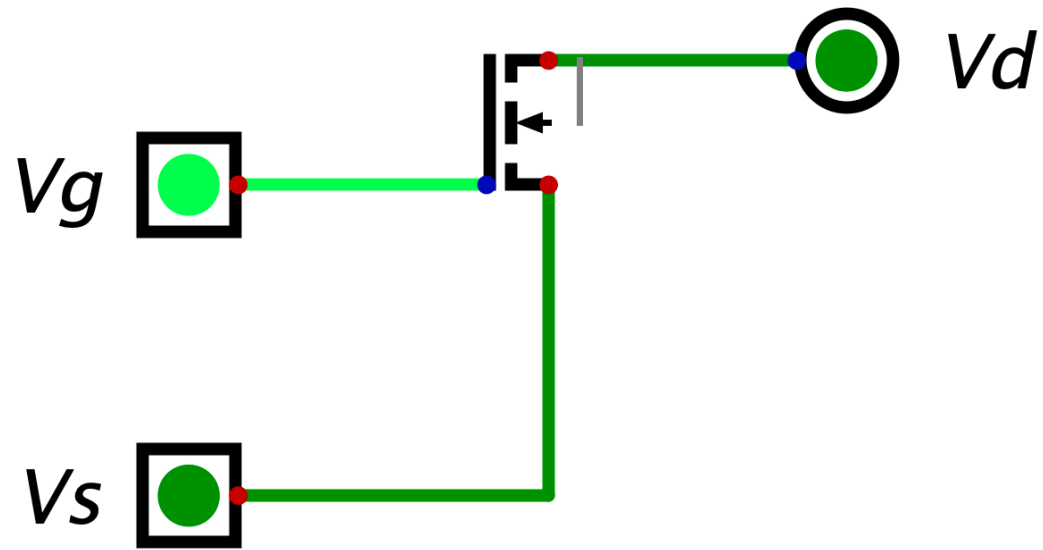
Dark green = Logic 0
Light green = Logic 1



Current **can** flow between the source and drain terminals because **V_g is high**


NMOS Transistor in “off” state

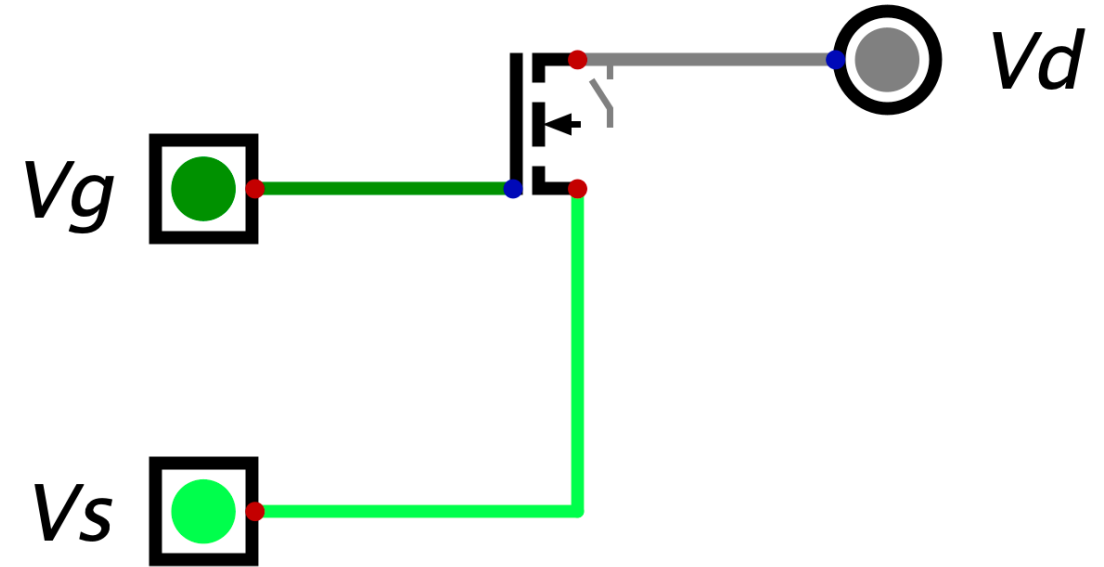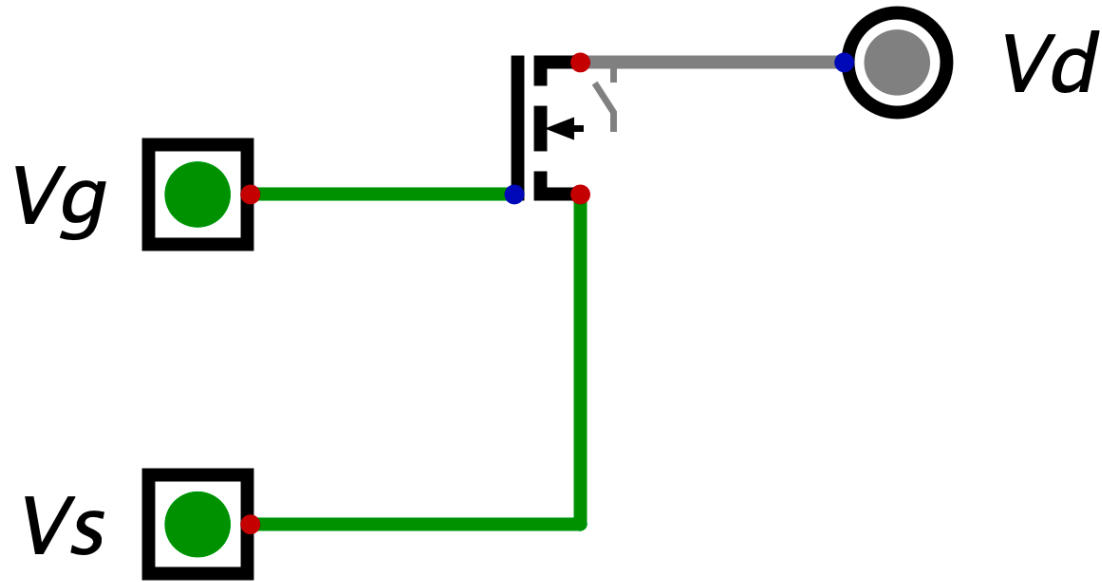Dark green = Logic 0
Light green = Logic 1




Current **cannot** flow between the source and drain terminals because **V_g is low**

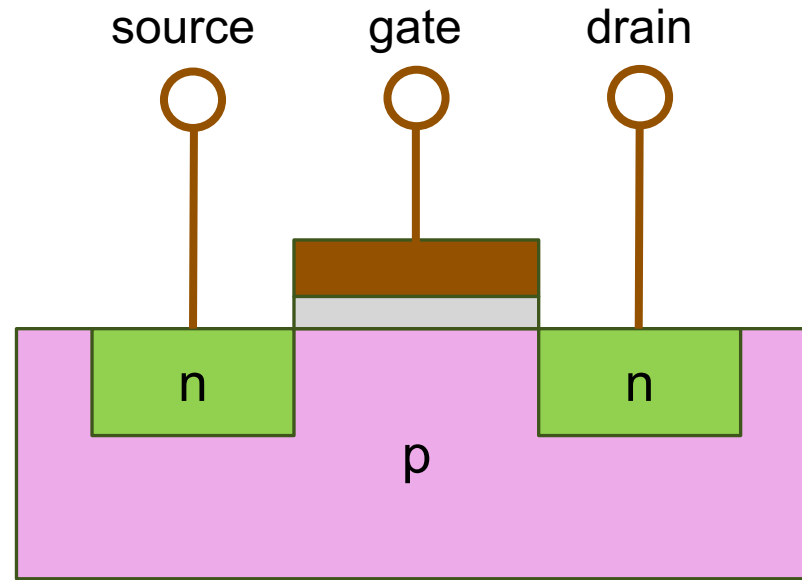n-channel Metal-Oxide-Semiconductor-Field-Effect Transistor (MOSFET)



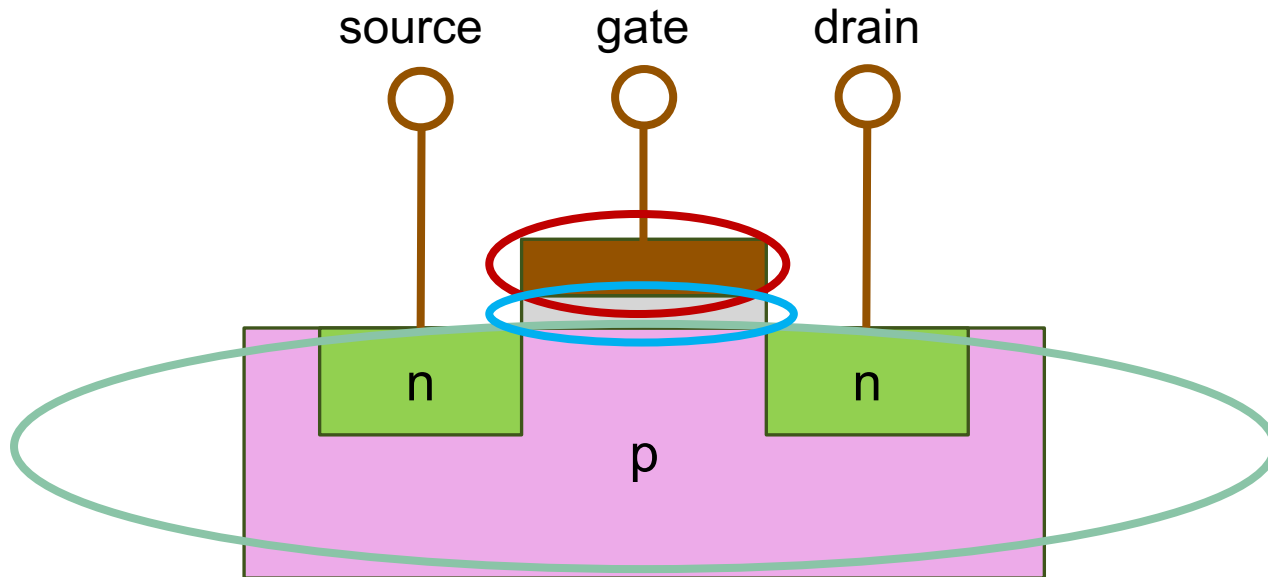n-channel Metal-Oxide-Semiconductor-Field-Effect Transistor (MOSFET)



Metal

material with high electrical conductivity


Oxide

insulates the semiconductor from the metal layer, forming a capacitor structure


Semiconductor

a material with an electrical conductivity between an insulator and conductor

n-channel MOSFET (nMOS)

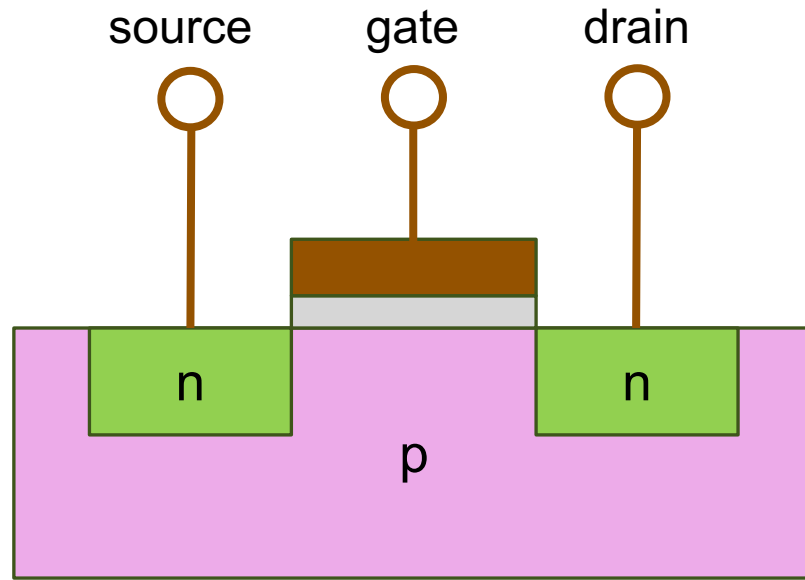


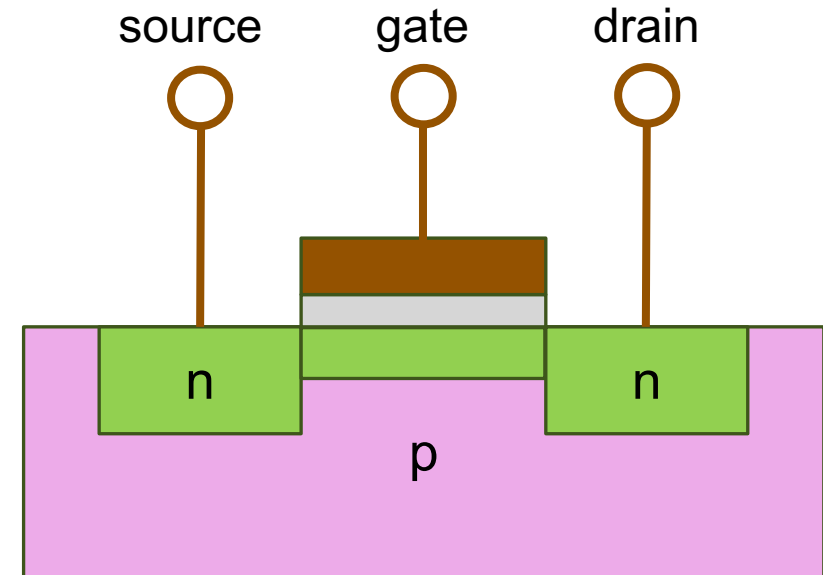V_g (gate voltage) = logic low
current **cannot** flow between source and drain





V_g (gate voltage) = logic high
current **can** flow between source and drain

Two Types of Transistors

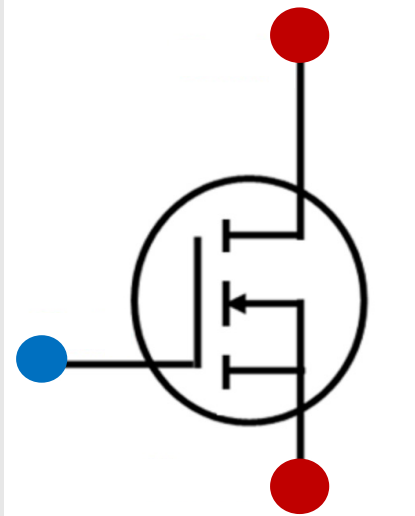	nMOS	pMOS
		
Behaves as an open switch when	V_g is low	
Behaves as a closed switch when	V_g is high	


V_g is the gate voltage (voltage on the blue terminal)

Two Types of Transistors

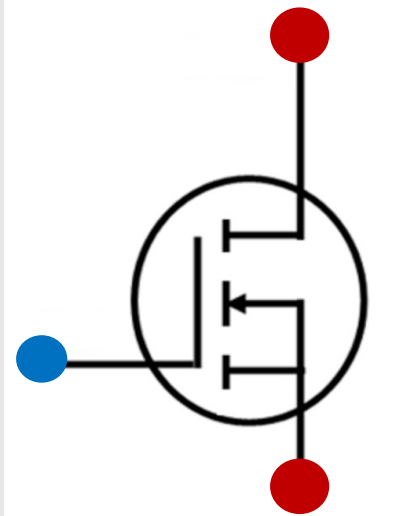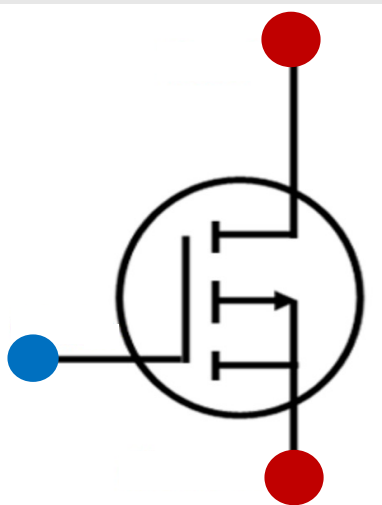	nMOS	pMOS
		
Behaves as an open switch when	V_g is low	V_g is high
Behaves as a closed switch when	V_g is high	V_g is low



V_g is the voltage on the blue terminal

PMOS Transistor

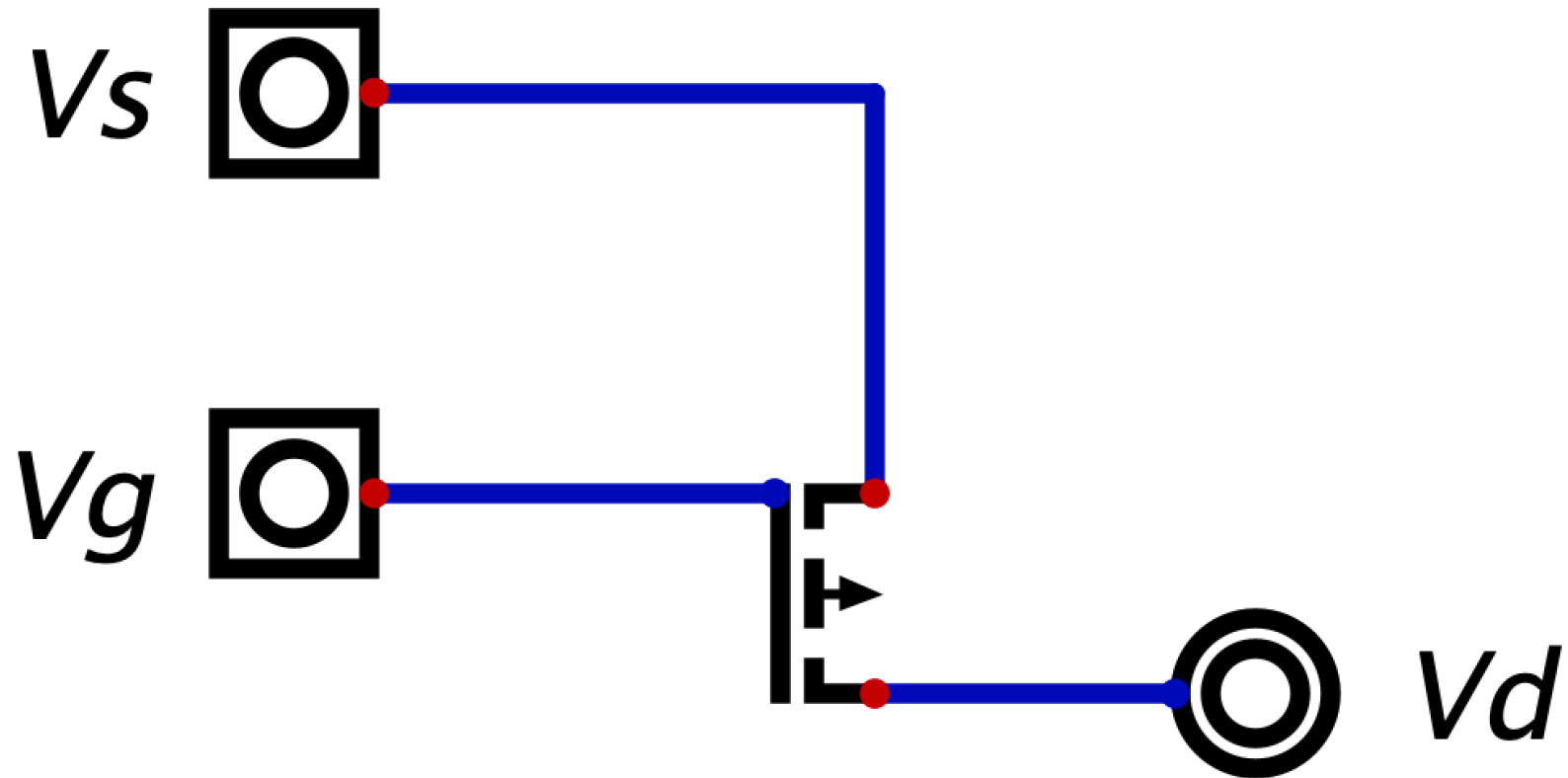

PMOS Transistor in “on” state

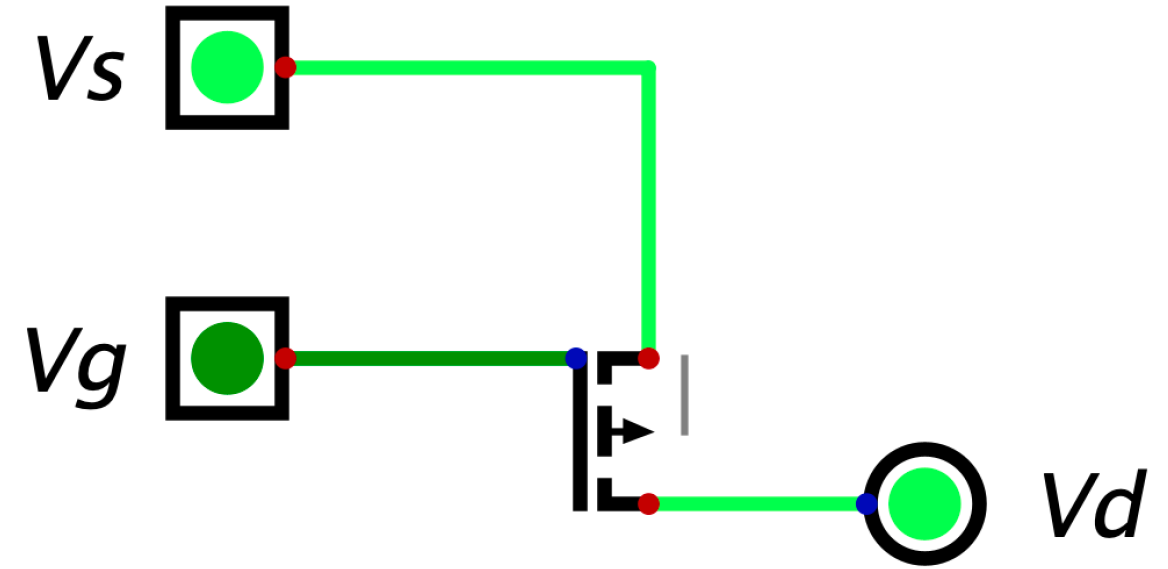
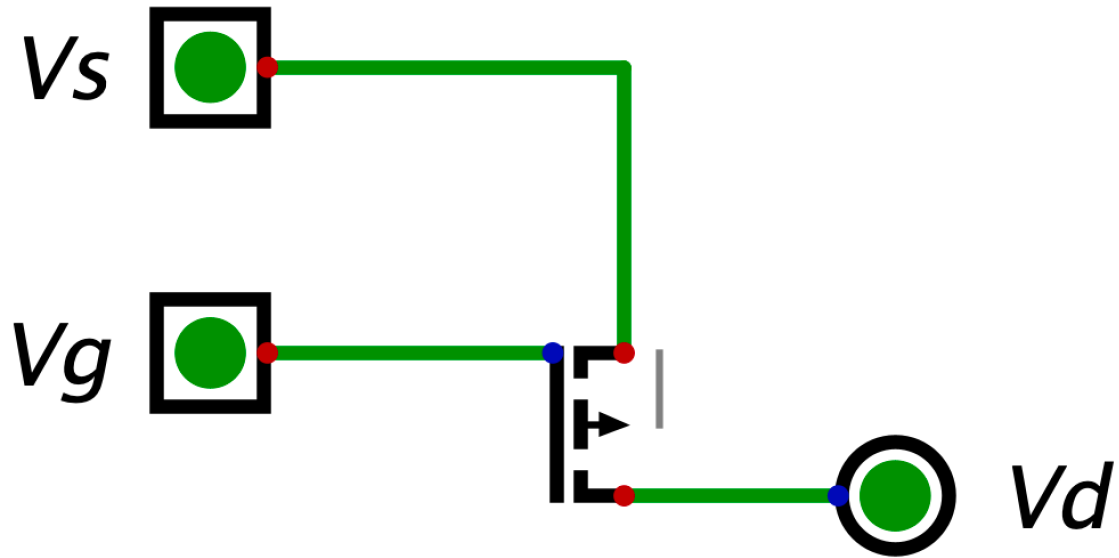
Dark green = Logic 0
Light green = Logic 1



Current **can** flow between the source and drain terminals because **V_g is low**


PMOS Transistor in “off” state

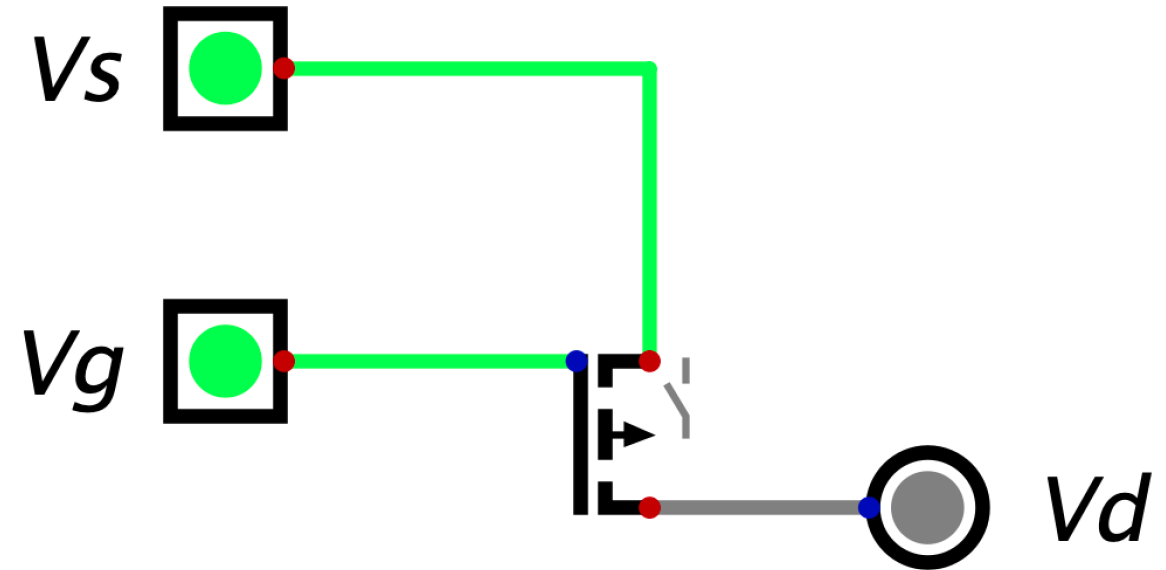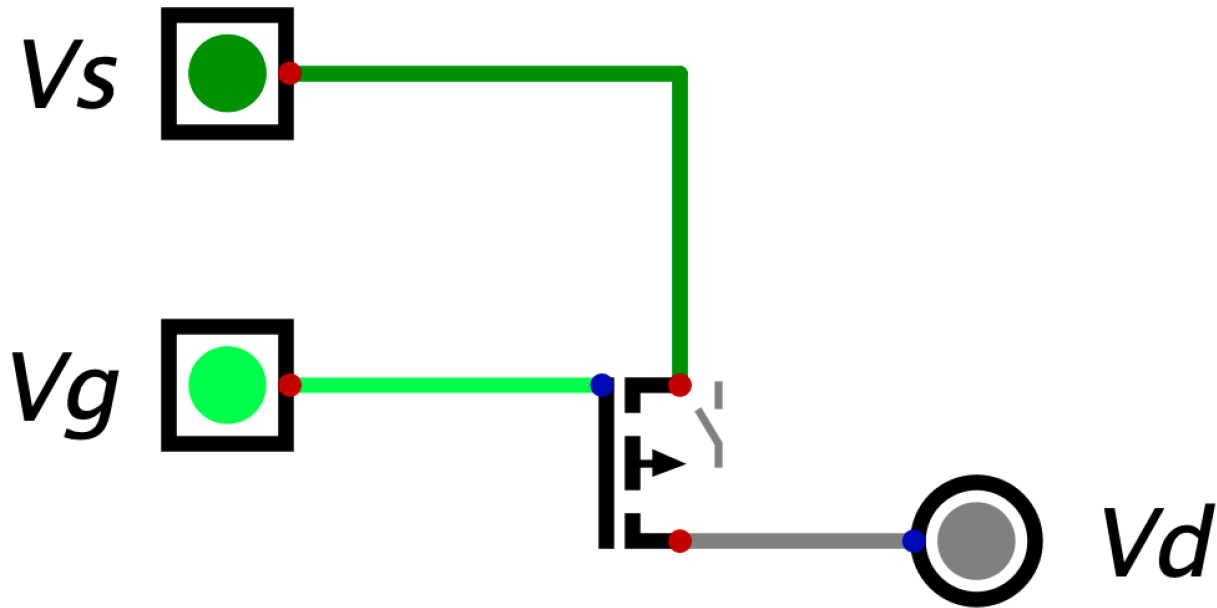Dark green = Logic 0
Light green = Logic 1




Current **cannot** flow between the source and drain terminals because **V_g is high**

Recall: Logic Levels

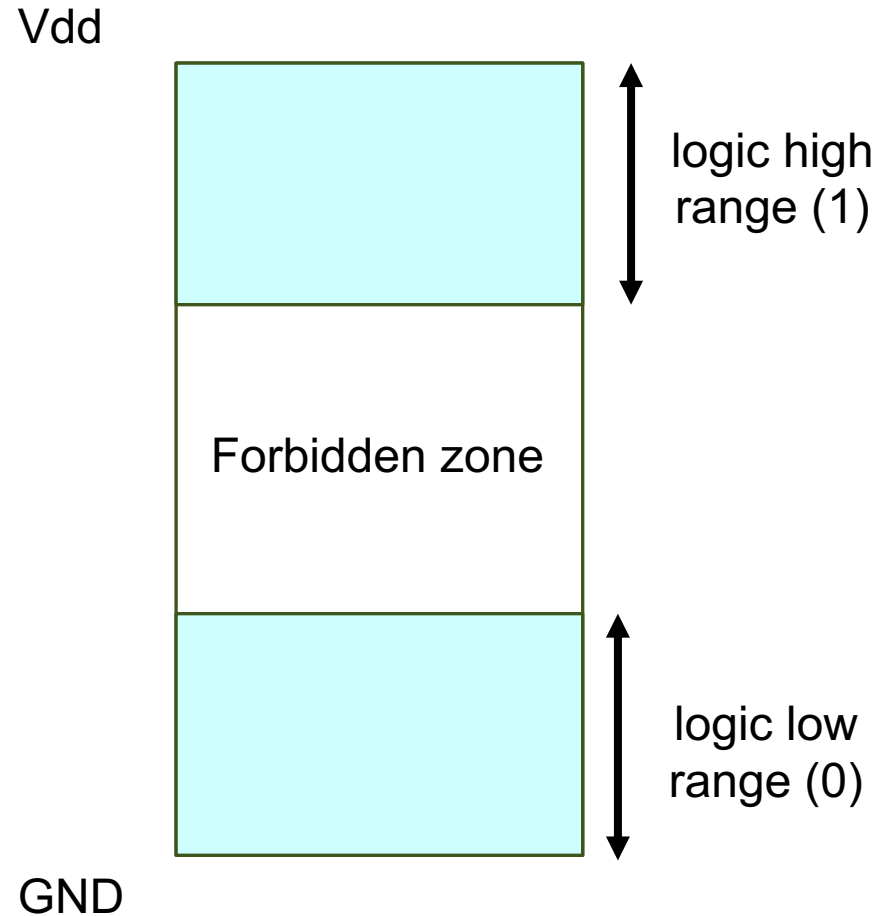


The exact voltage ranges are determined by the characteristics of the transistor

Comparing Logic High Outputs

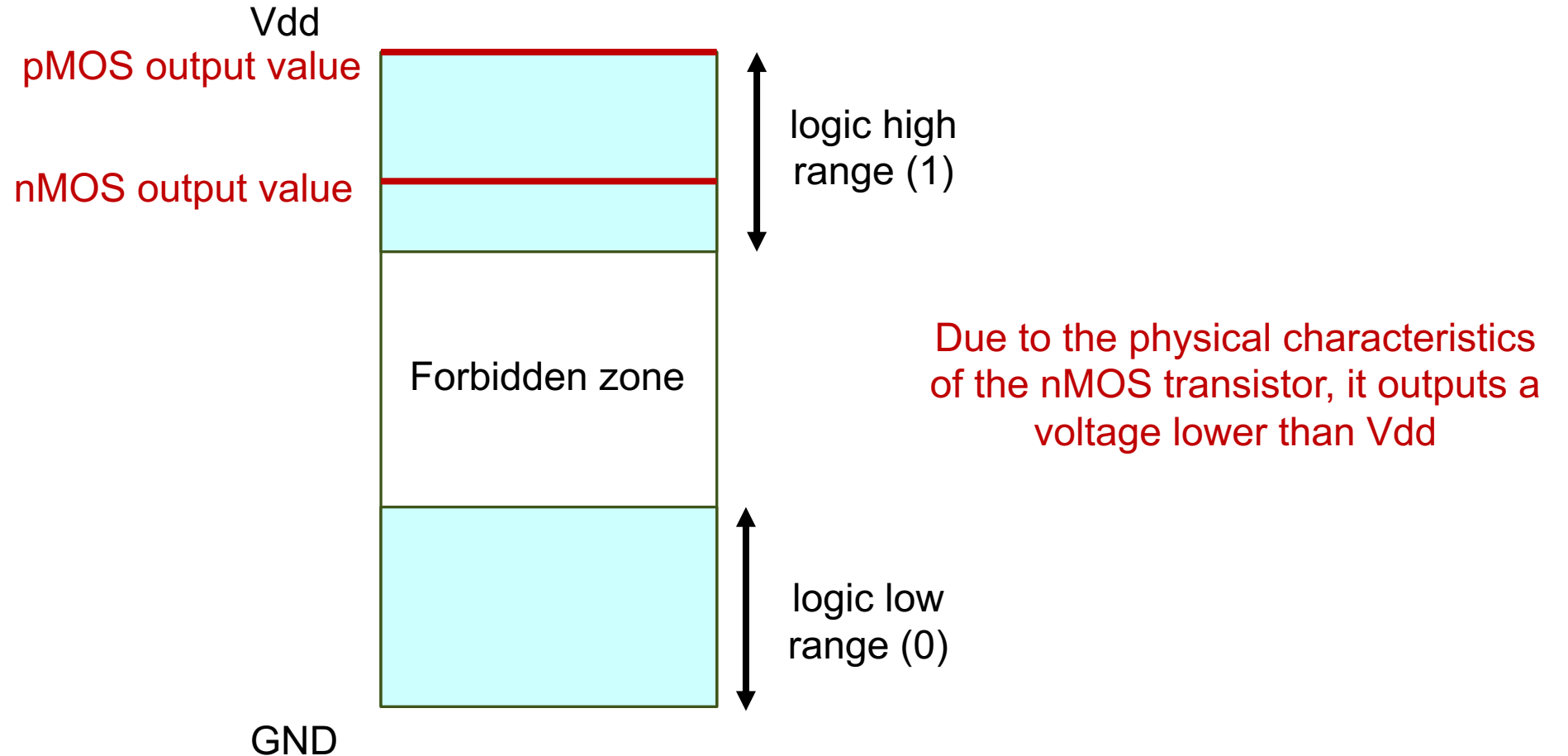

The exact voltage ranges are determined by the characteristics of the transistor



Comparing Logic Low Outputs

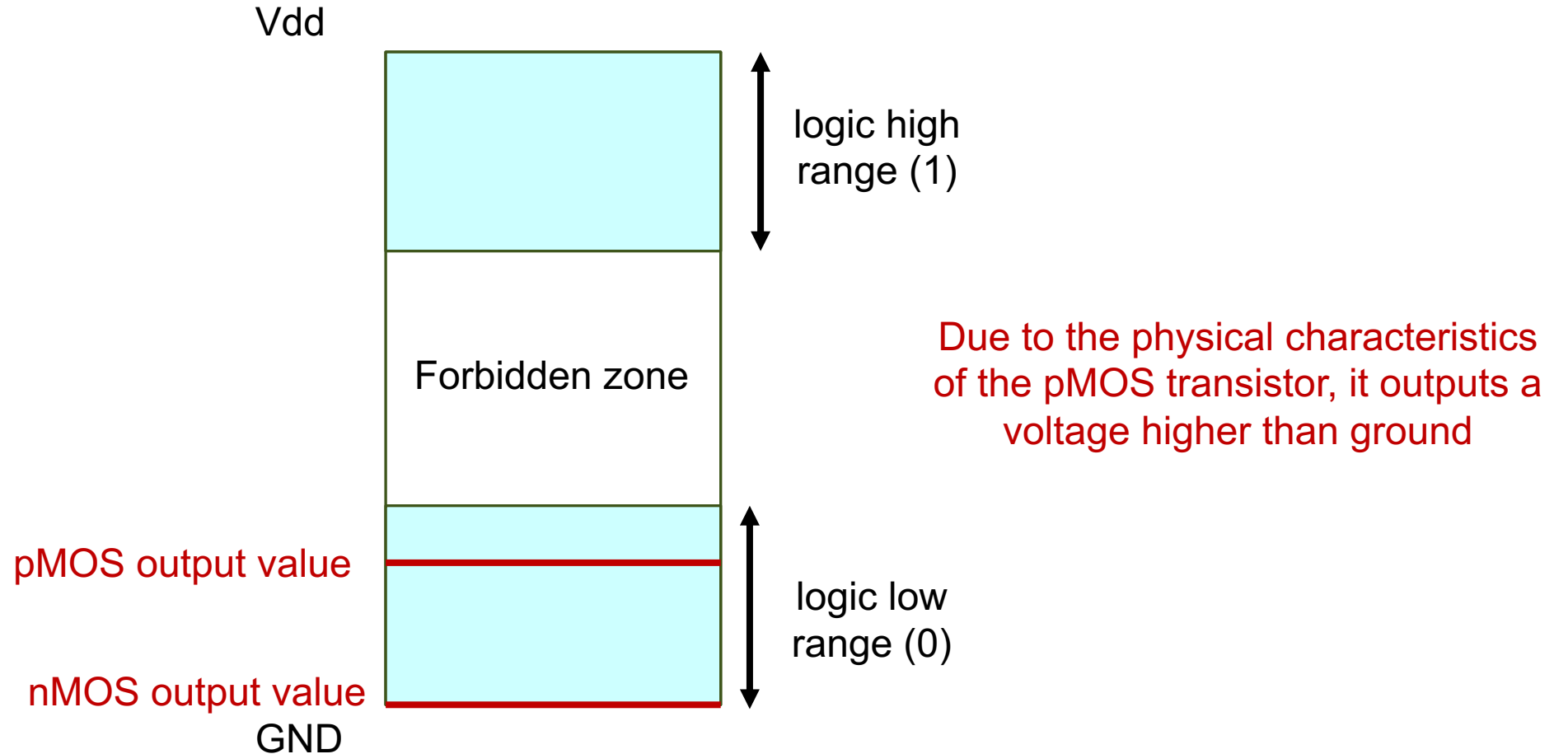

The exact voltage ranges are determined by the characteristics of the transistor

NMOS Transistor in “on” state

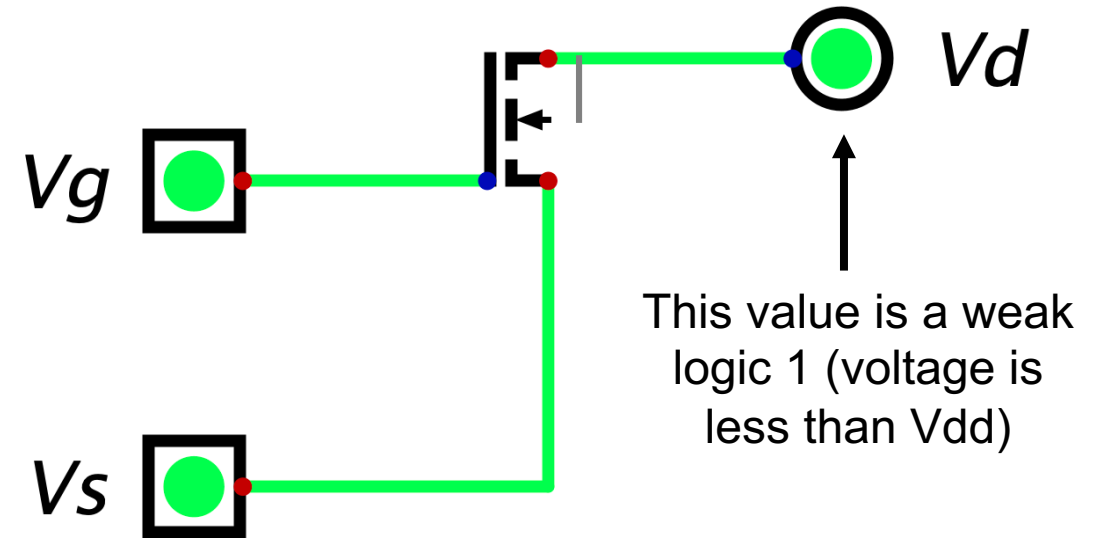
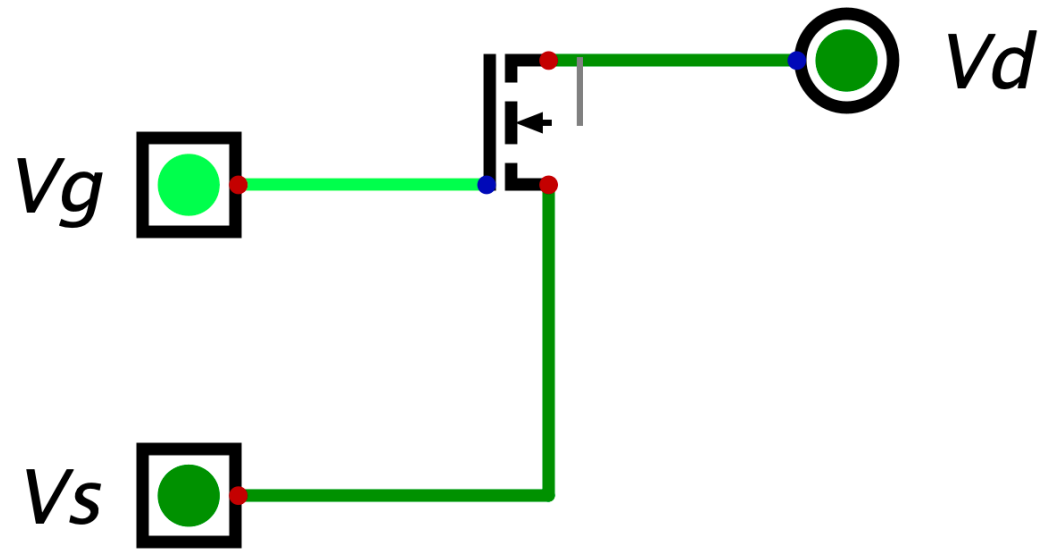
Dark green = Logic 0
Light green = Logic 1



Current **can** flow between the source and drain terminals because **V_g is high**

NMOS Transistor in “off” state

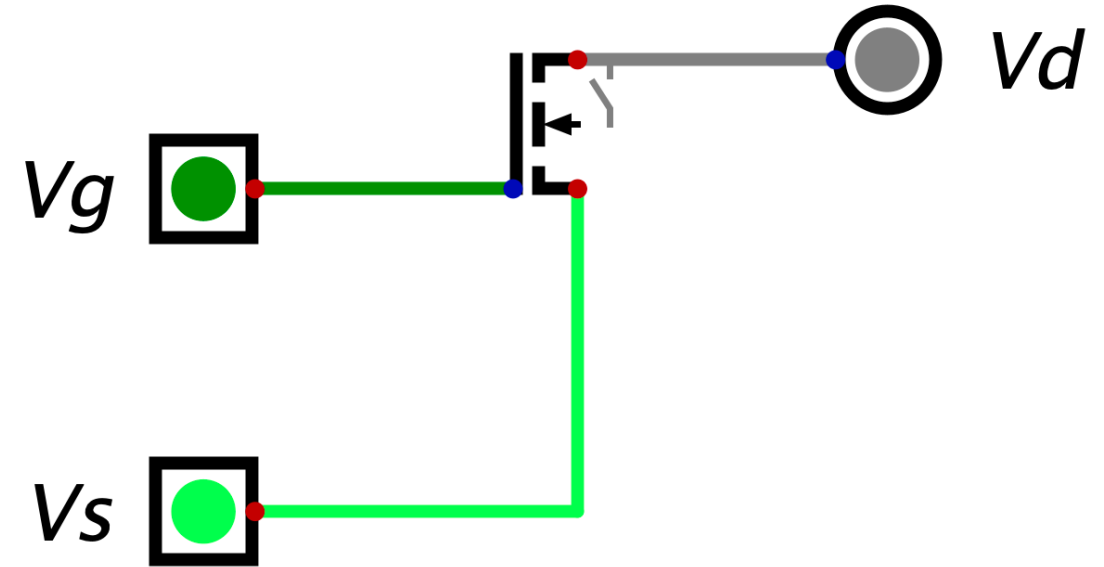
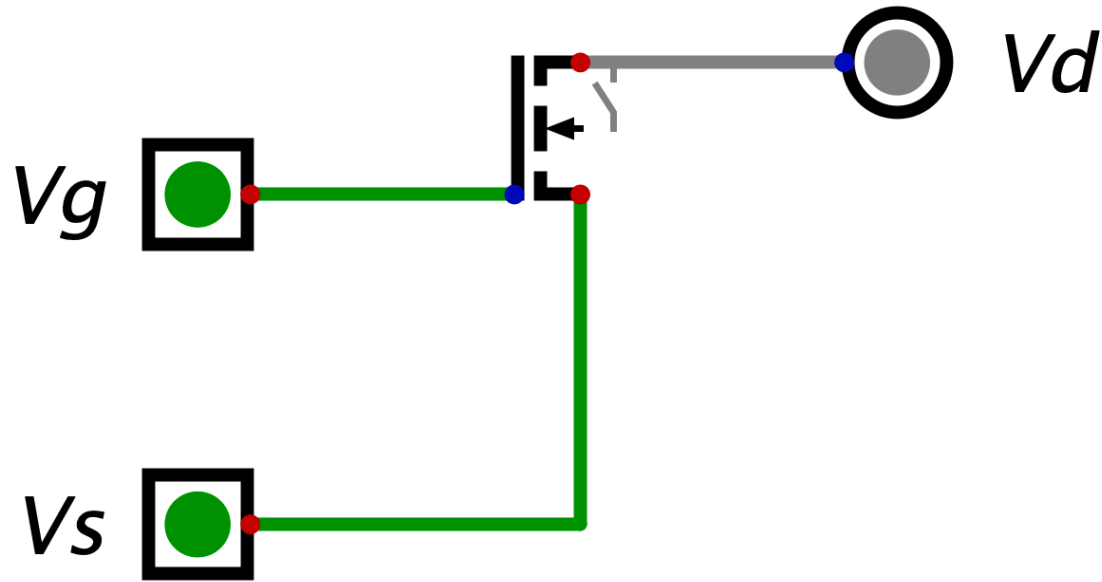
Dark green = Logic 0
Light green = Logic 1



Current **cannot** flow between the source and drain terminals because **V_g is low**

PMOS Transistor in “on” state

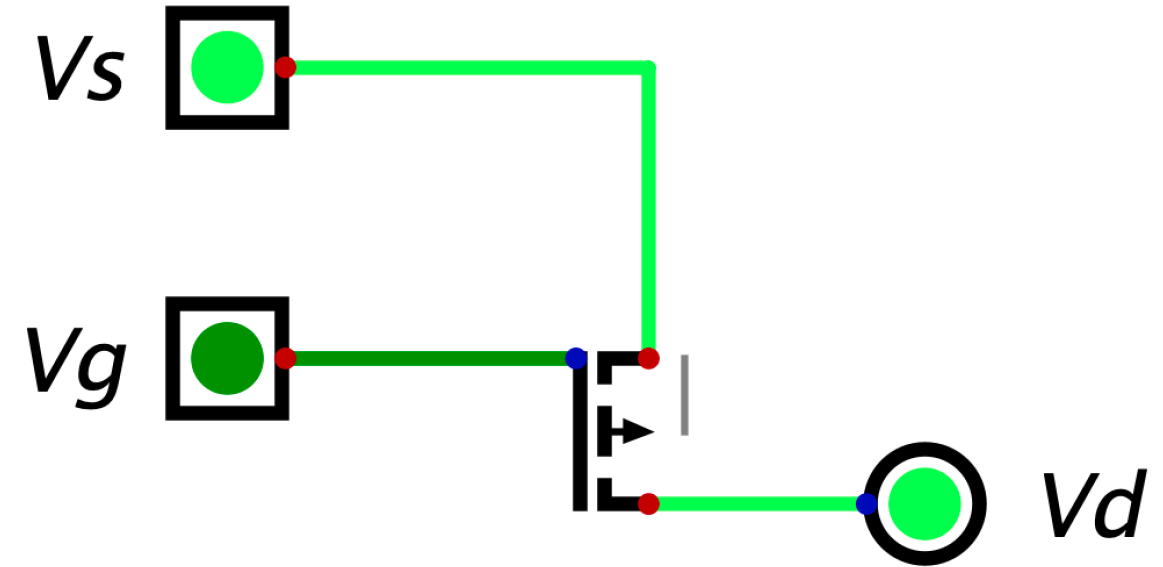
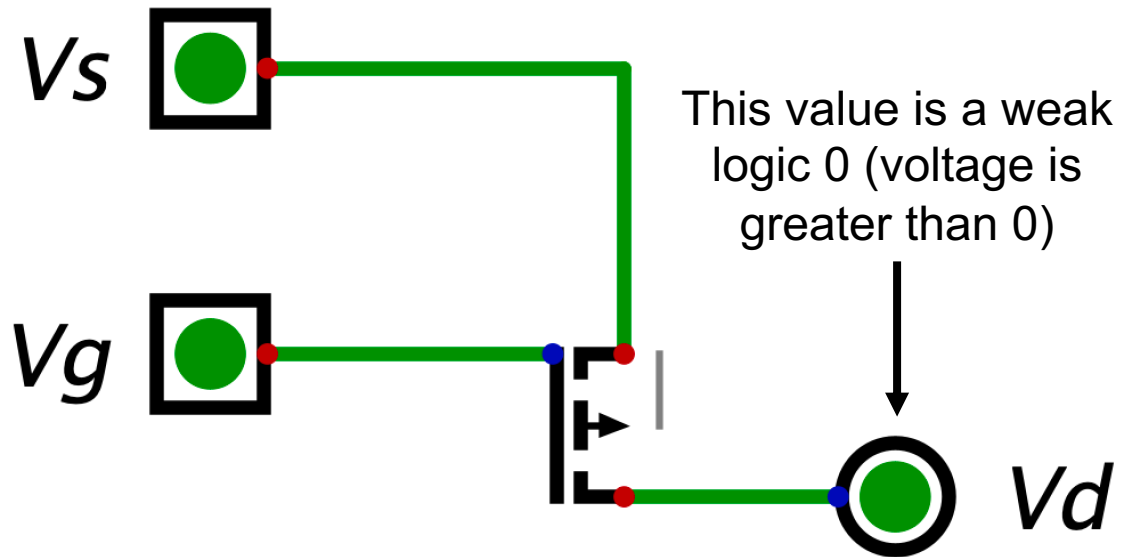
Dark green = Logic 0
Light green = Logic 1



Current **can** flow between the source and drain terminals because **V_g is low**

PMOS Transistor in “off” state

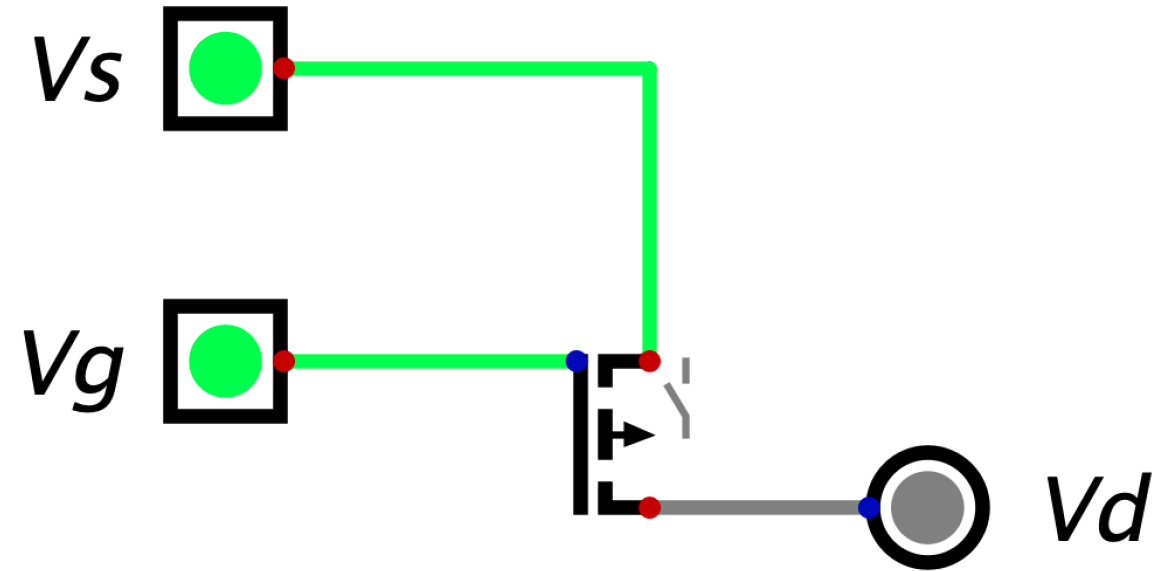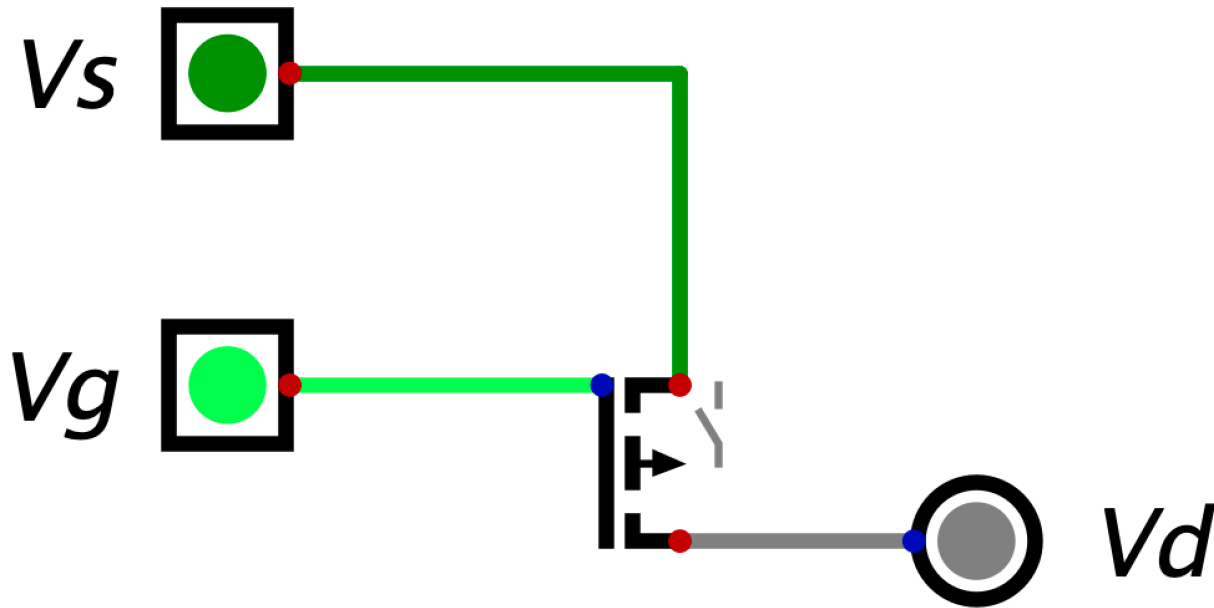Dark green = Logic 0
Light green = Logic 1



Current **cannot** flow between the source and drain terminals because **V_g is high**

nMOS vs pMOS


Characteristic	nMOS	pMOS
$V_g = 1$	on	off
$V_g = 0$	off	on
Which signal is passed well	low	high
Symbol	arrow facing in	arrow facing out

Designing An Inverter

- I want to design a circuit that takes as an input a one-bit value and outputs the complement of that number.
 - Input = 0, Output = 1
 - Input = 1, Output = 0
- I want to avoid having weak outputs.


Designing An Inverter

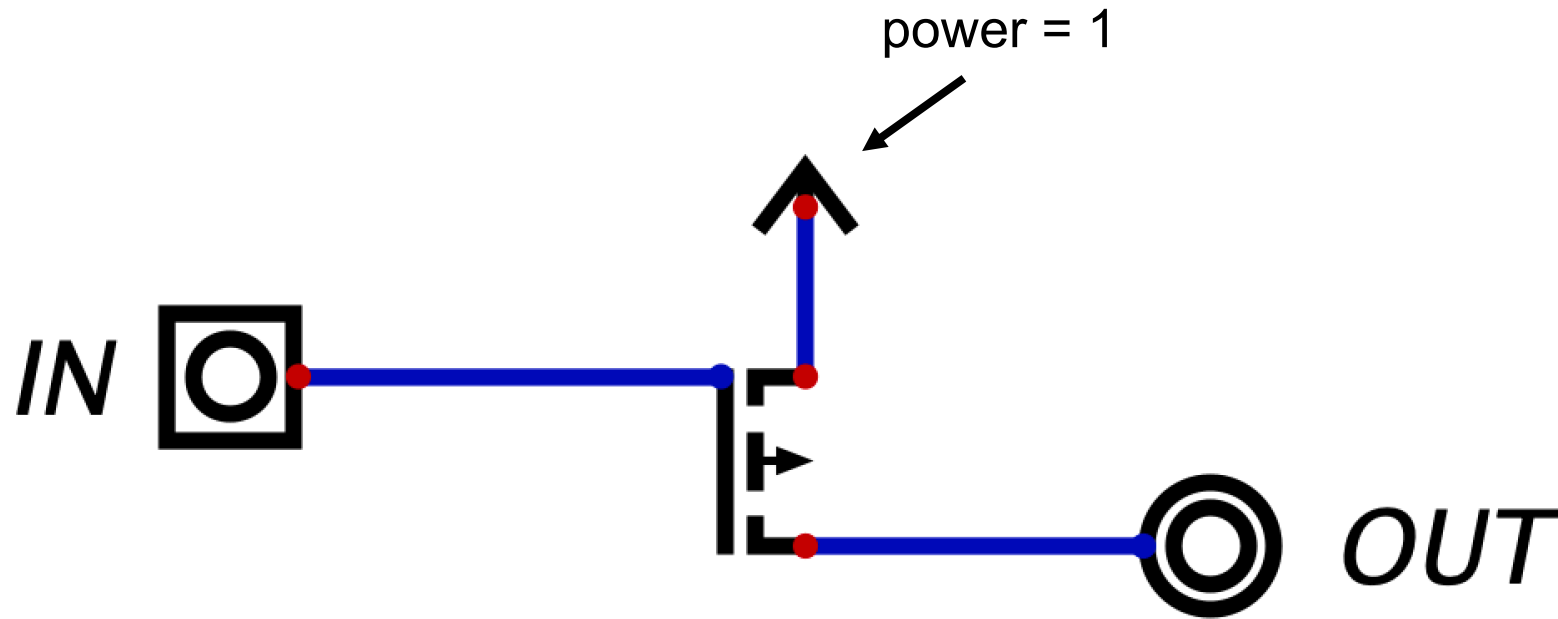We will use a **PMOS** transistor to drive the output when the **input is 0**.




Designing An Inverter

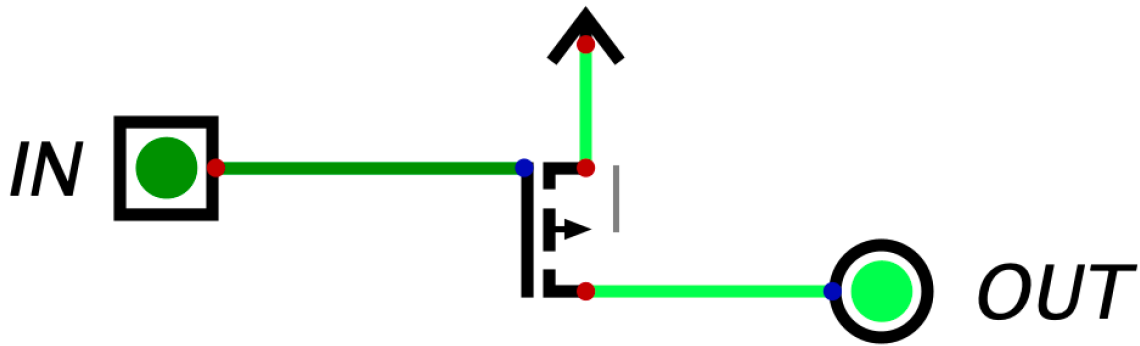We will use a **PMOS** transistor to drive the output when the **input is 0**.




When the input is 0, the output is 1

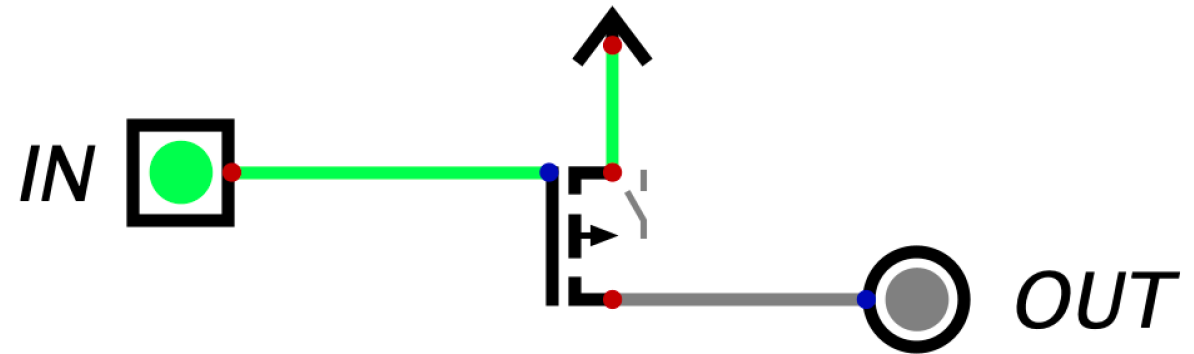

When the input is 1, the output is not connected


Designing An Inverter

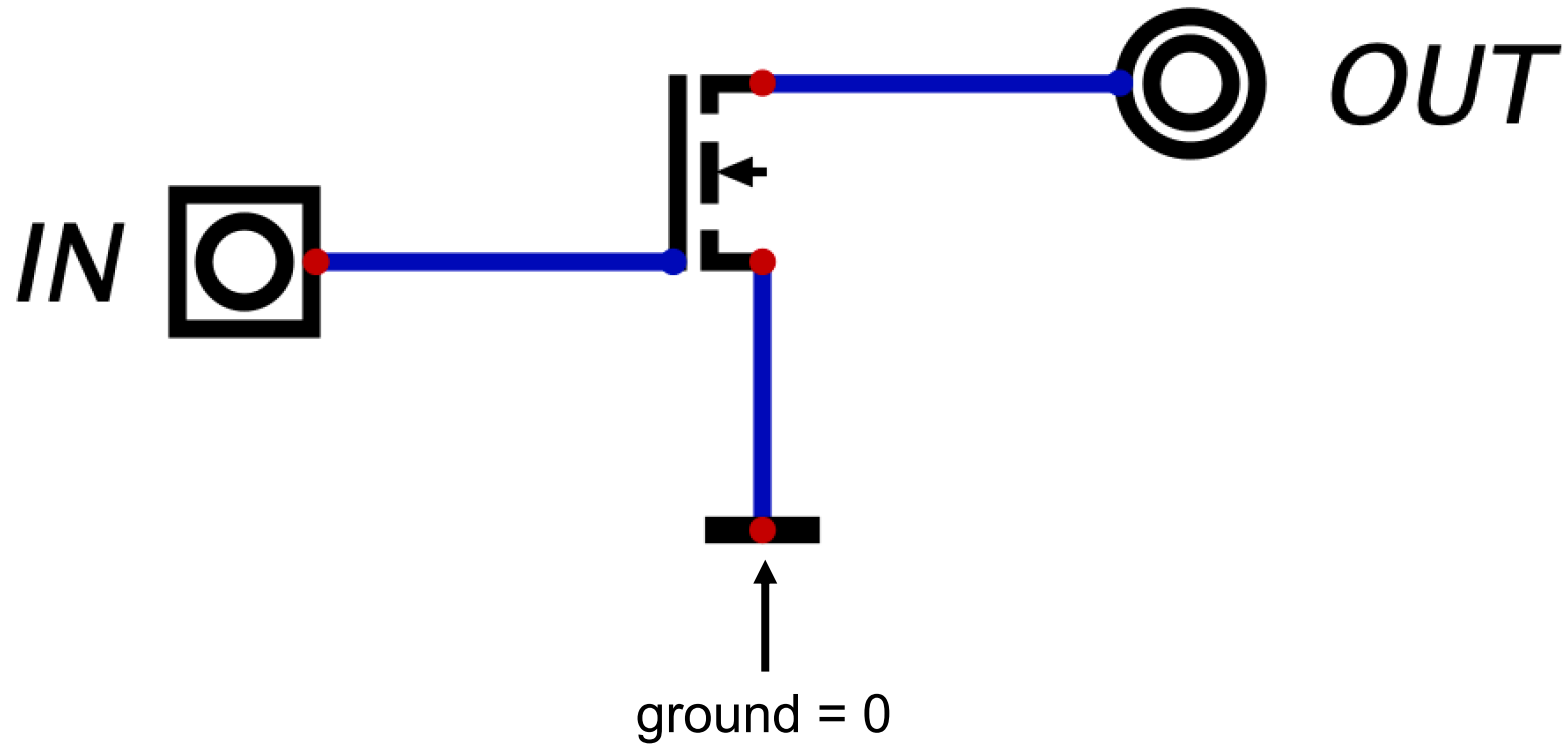We will use an **NMOS** transistor to drive the output when the **input is 1**.




Designing An Inverter

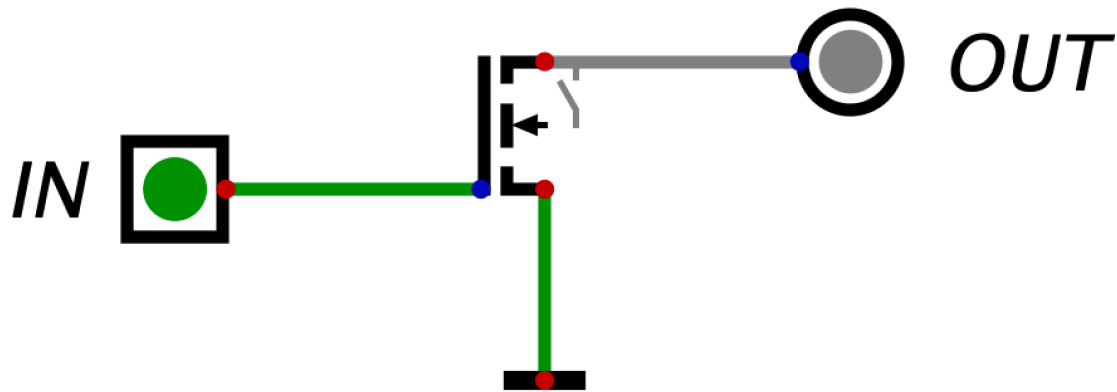We will use an **NMOS** transistor to drive the output when the **input is 1**.



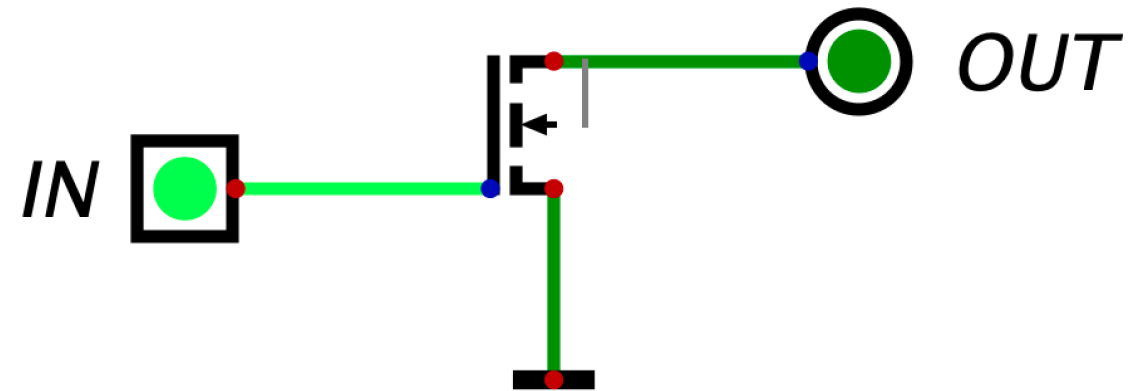
When the input is 0, the output is not connected



When the input is 1, the output is 0


CMOS (Complementary Metal Oxide Semiconductor) Inverter

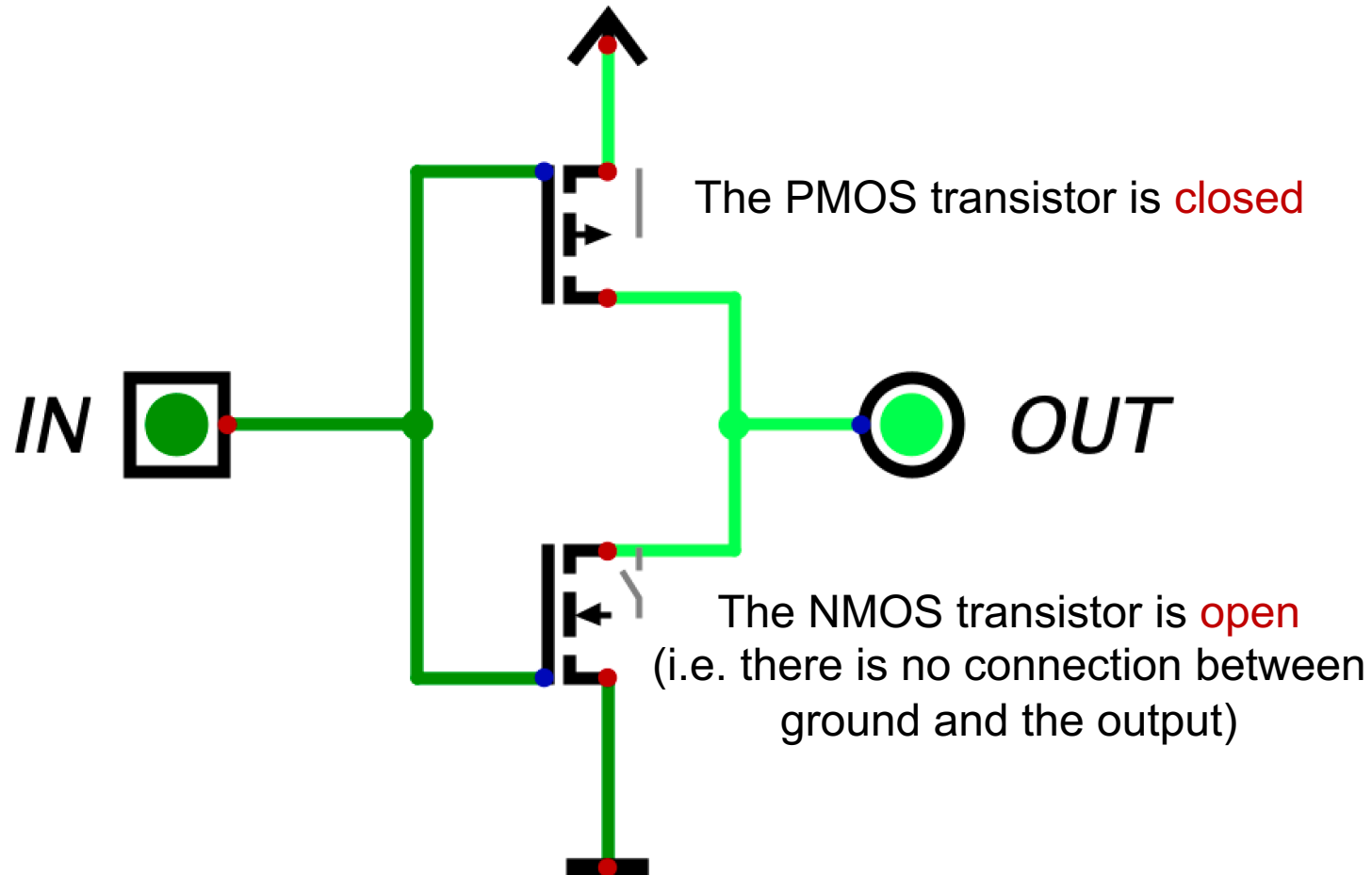When the input is 0, power is connected to the output




CMOS Inverter

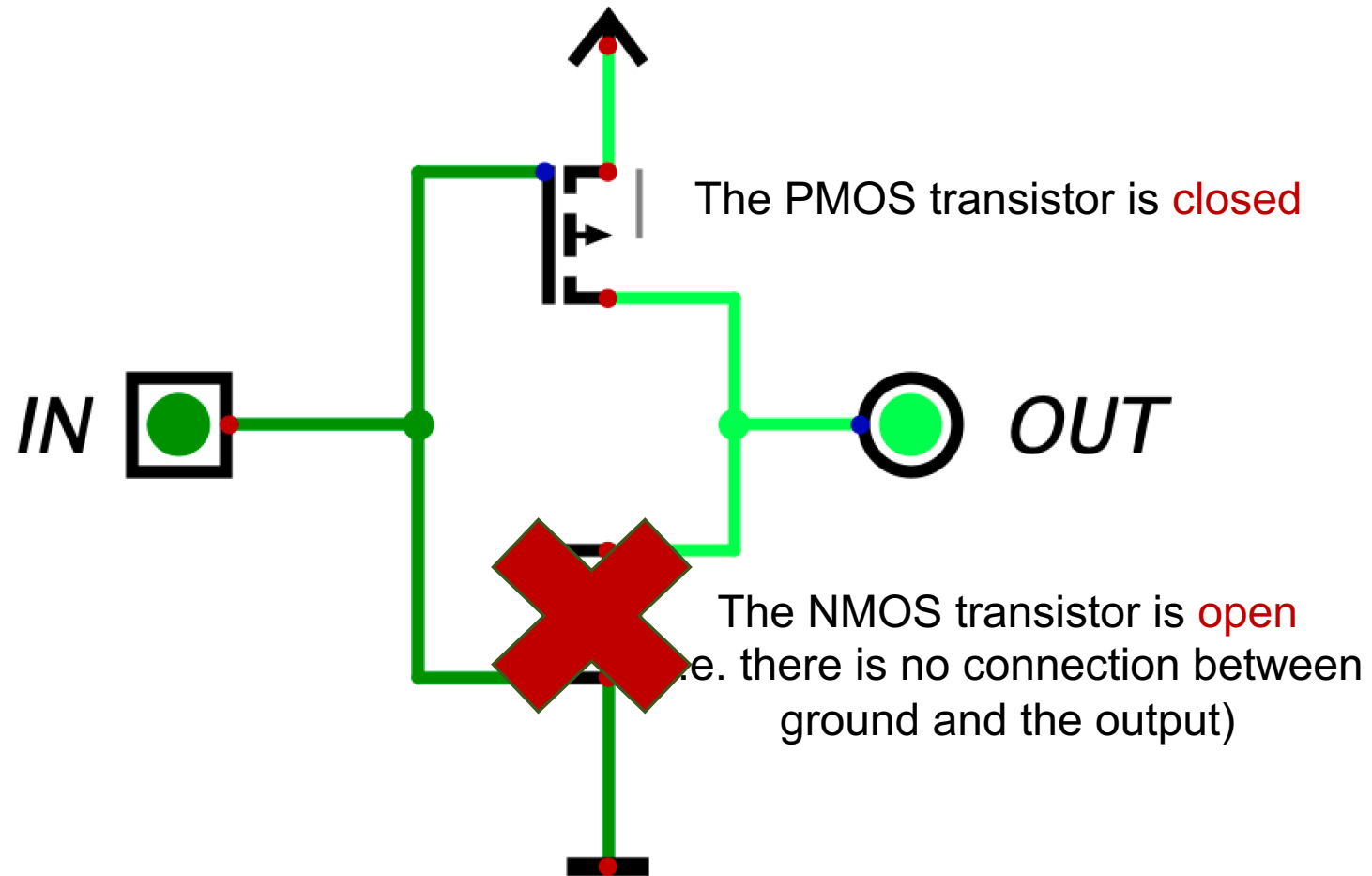When the input is 0, power is connected to the output




CMOS Inverter

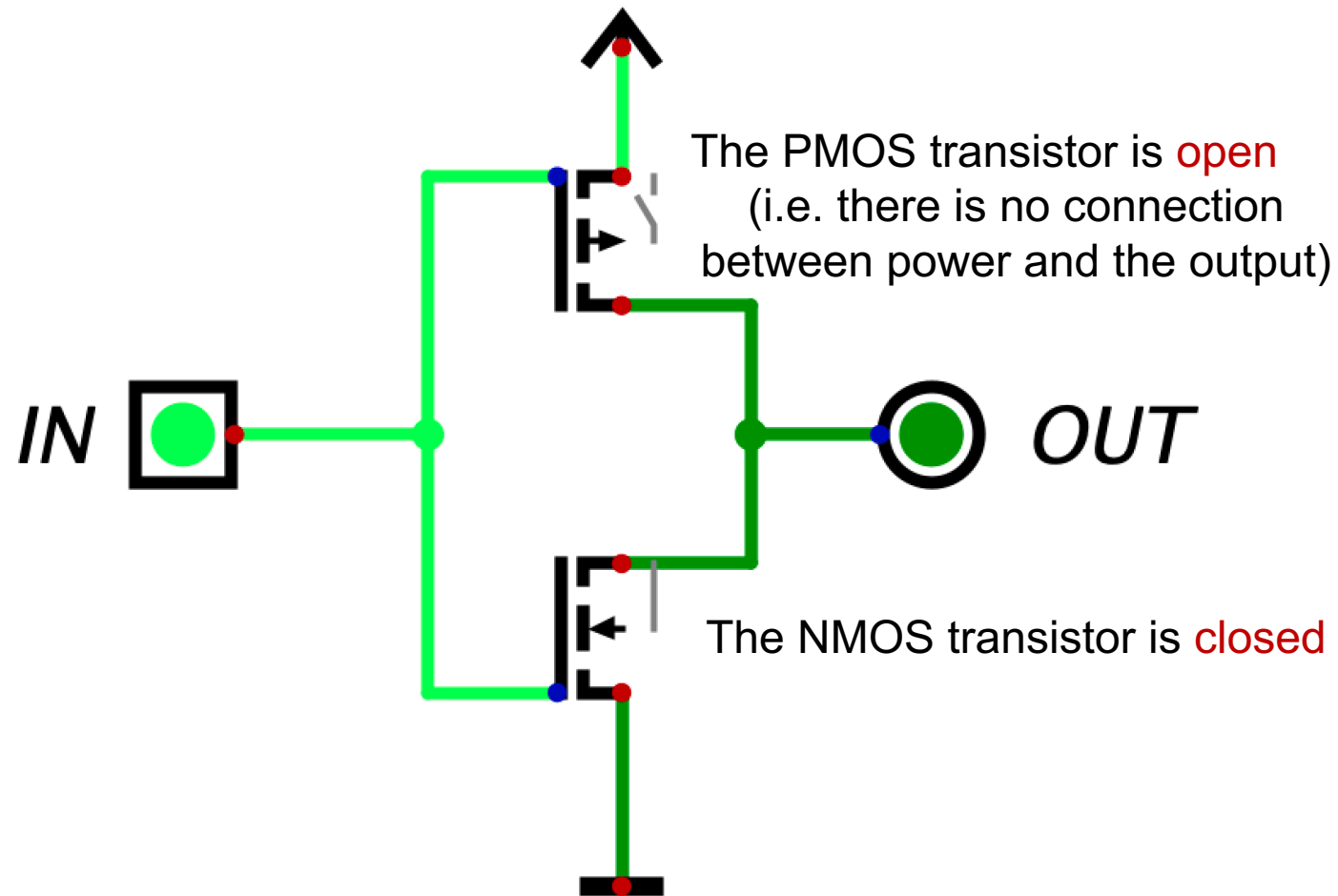When the input is 1, ground is connected to the output




CMOS Inverter

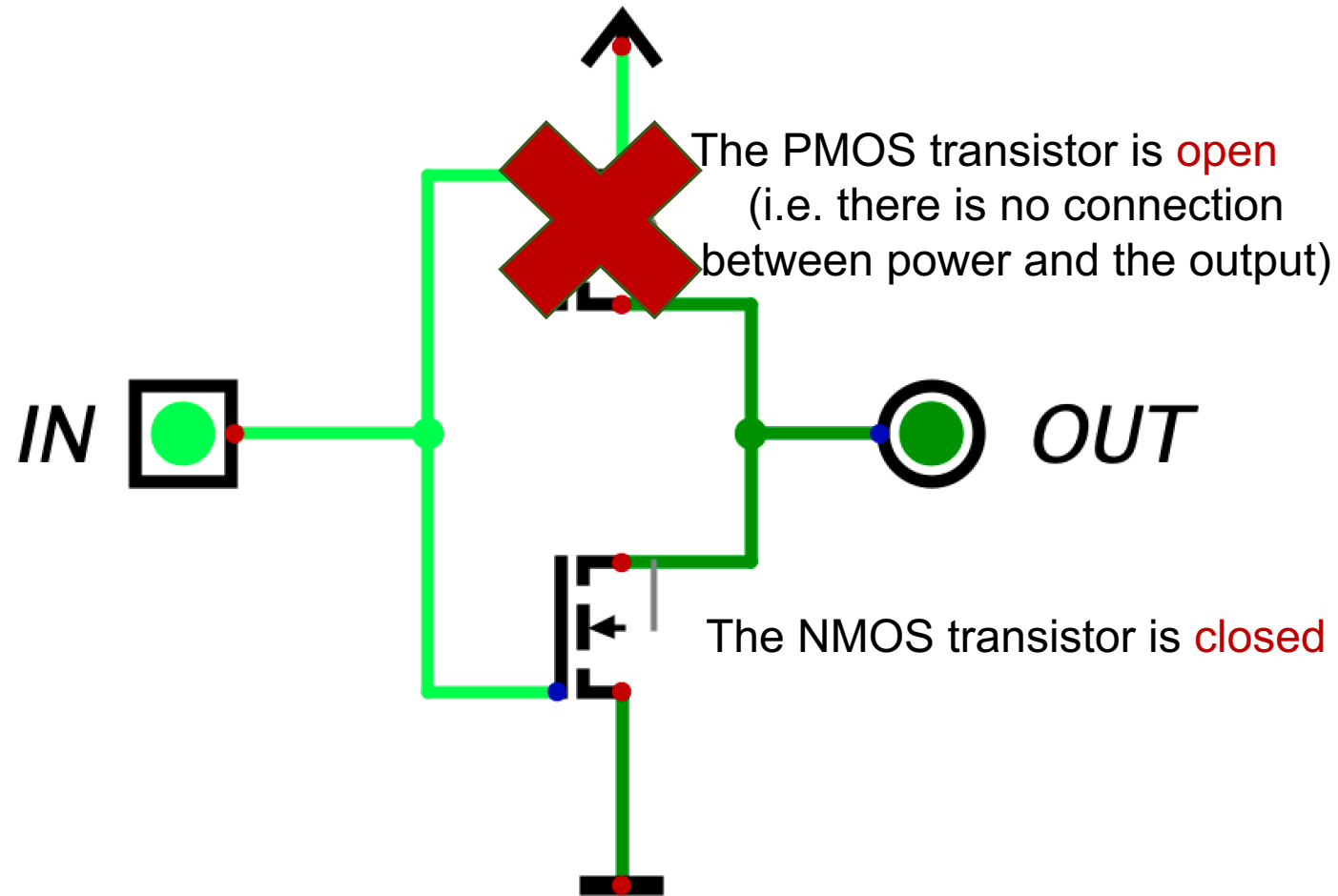When the input is 1, ground is connected to the output




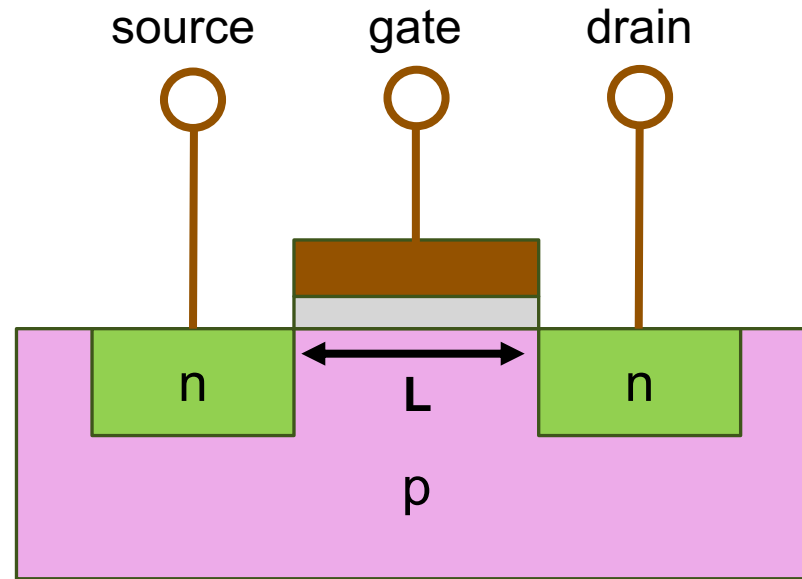n-channel Metal-Oxide-Semiconductor-Field-Effect Transistor (MOSFET)



L = length of the channel


Transistor Size

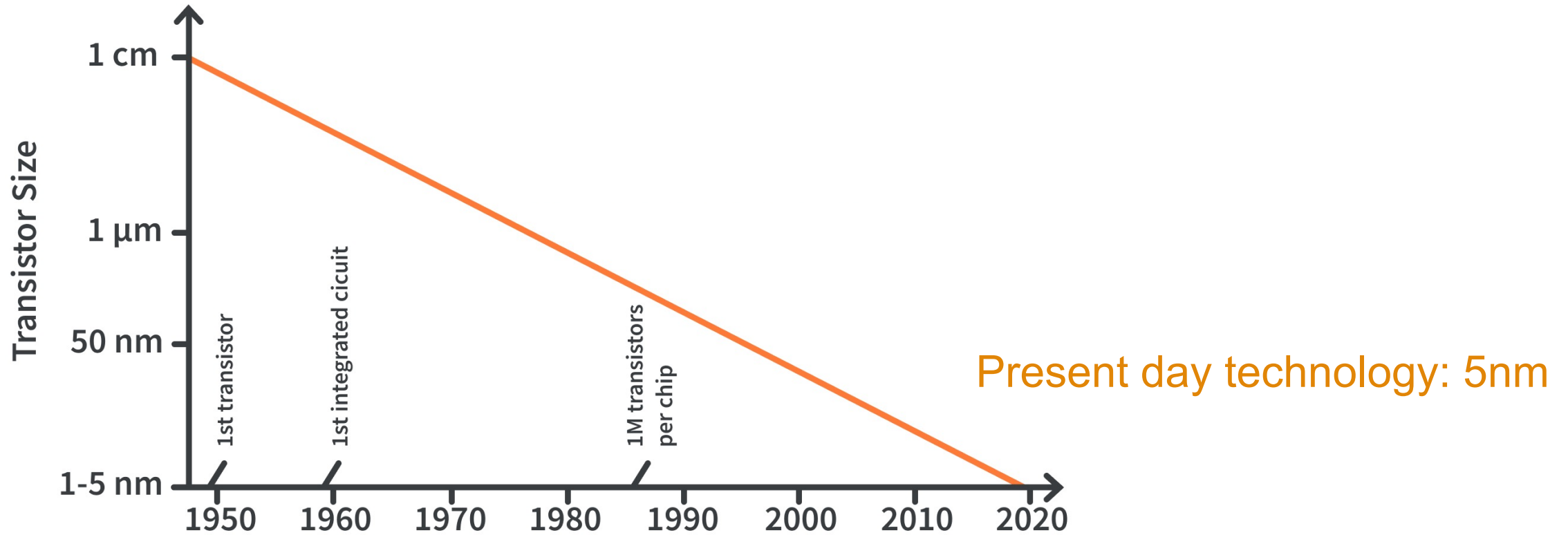

Transistor Size

Present day technology: 5nm

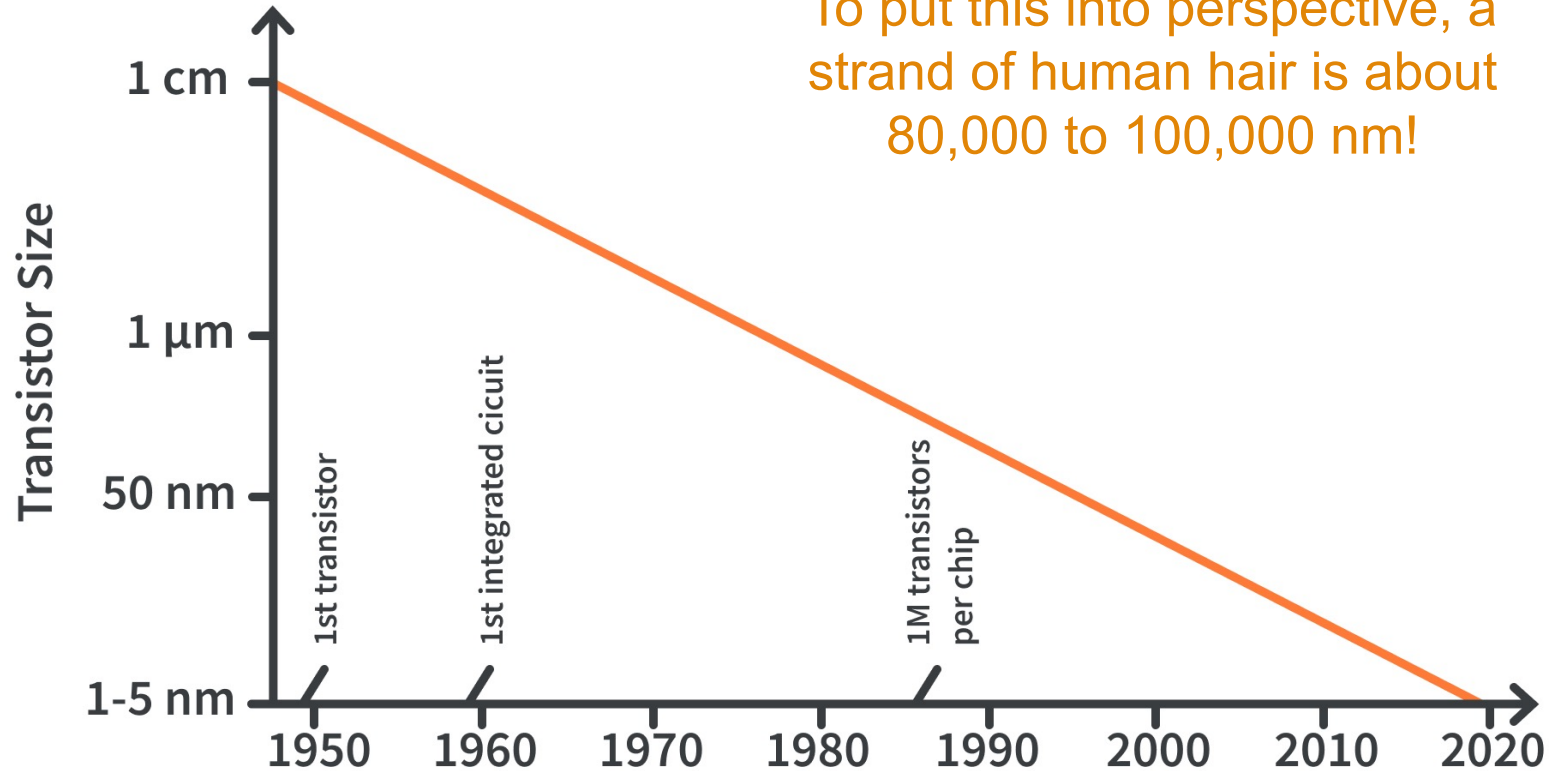To put this into perspective, a strand of human hair is about 80,000 to 100,000 nm!



As transistor size decreases, speed increases

Moore's Law

Moore's Law: The number of transistors on microchips doubles every two years

Moore's law describes the empirical regularity that the number of transistors on integrated circuits doubles approximately every two years. This advancement is important for other aspects of technological progress in computing – such as processing speed or the price of computers.

Our World
in Data

Transistor count

50,000,000,000

10,000,000,000

5,000,000,000

1,000,000,000

500,000,000

100,000,000

50,000,000

10,000,000

5,000,000

1,000,000

500,000

100,000

50,000

10,000

5,000

1,000

1970 1972 1974 1976 1978 1980 1982 1984 1986 1988 1990 1992 1994 1996 1998 2000 2002 2004 2006 2008 2010 2012 2014 2016 2018 2020

Data source: Wikipedia (wikipedia.org/wiki/Transistor_count)

OurWorldinData.org – Research and data to make progress against the world's largest problems.

Licensed under CC-BY by the authors Hannah Ritchie and Max Roser.

Exponential growth!



Logic Gates



Inverter/Not Gate

Symbol



Truth Table

A	Y
0	
1	

Equation

Inverter/Not Gate

Symbol



Truth Table


A	Y
0	1
1	0

Equation

$$Y = \bar{A}$$

AND Gate

Symbol

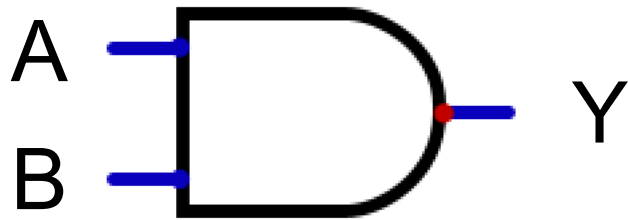


Truth Table

A	B	Y
0	0	
0	1	
1	0	
1	1	

Equation

AND Gate

Symbol

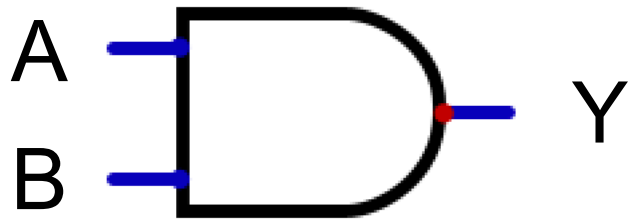

Truth Table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Equation


$$Y = A \times B$$

or

$$Y = AB$$

OR Gate

Symbol

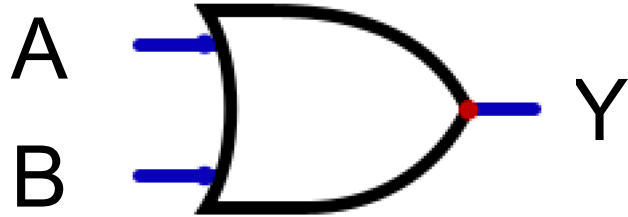


Truth Table

A	B	Y
0	0	
0	1	
1	0	
1	1	

Equation

OR Gate

Symbol

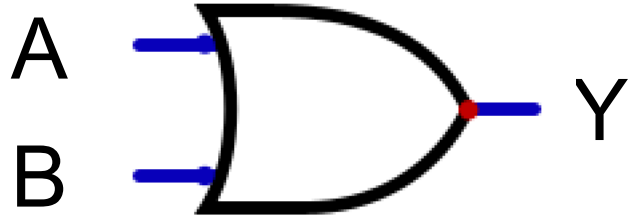

Truth Table


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Equation

$$Y = A + B$$

XOR Gate

Symbol

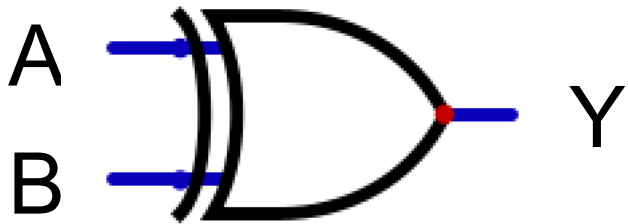


Truth Table

A	B	Y
0	0	
0	1	
1	0	
1	1	

Equation

XOR Gate

Symbol

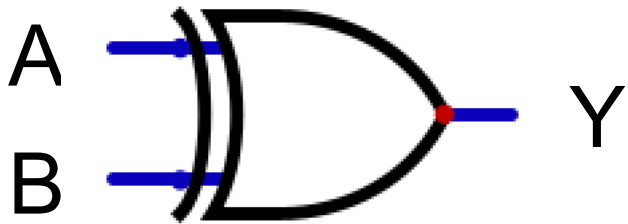

Truth Table


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Equation

$$Y = A \oplus B$$

NAND

Symbol

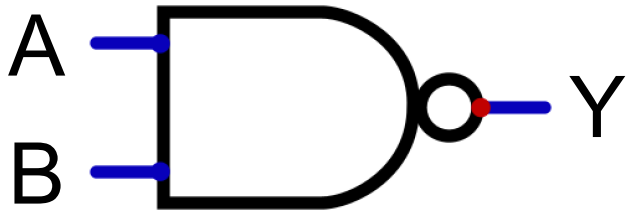


Truth Table

A	B	Y
0	0	
0	1	
1	0	
1	1	

Equation

NAND

Symbol

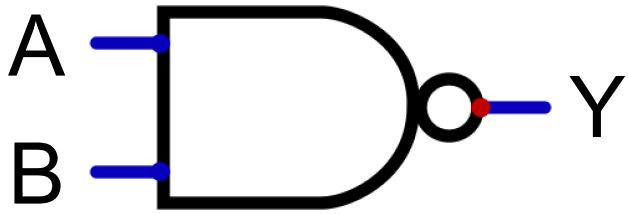

Truth Table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Equation


$$Y = \overline{A \times B}$$

or

$$Y = \overline{AB}$$

NOR

Symbol

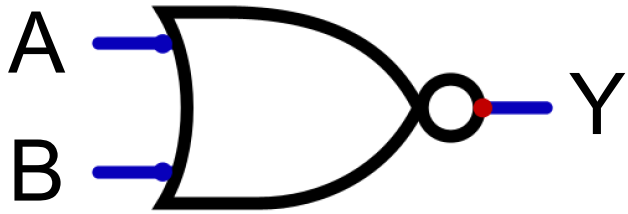


Truth Table

A	B	Y
0	0	
0	1	
1	0	
1	1	

Equation

NOR

Symbol

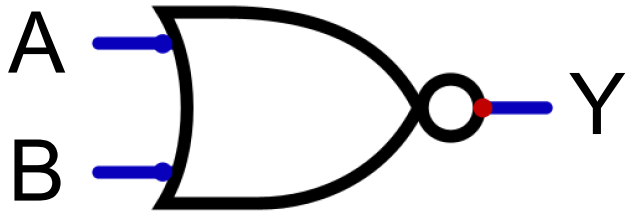

Truth Table


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Equation

$$Y = \overline{A + B}$$

XNOR Gate

Symbol

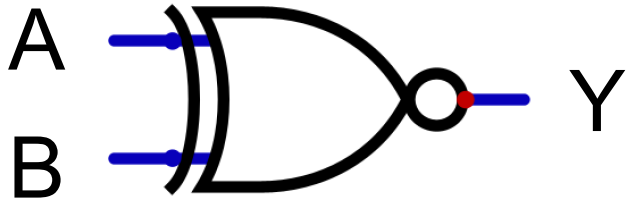


Truth Table

A	B	Y
0	0	
0	1	
1	0	
1	1	

Equation

XNOR Gate

Symbol

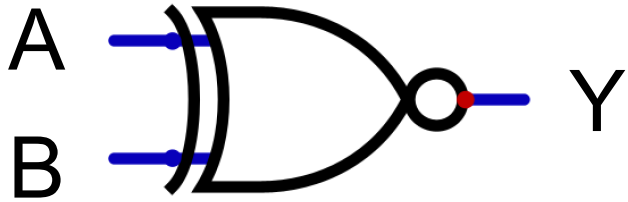

Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Equation

$$Y = \overline{A \oplus B}$$